

CS39001 - COMPUTER ORGANIZATION LABORATORY

INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Verilog Assignment 1

Authors:

Ashish Rekhani (ID: 20CS10010)

Kartik Pontula (ID: 20CS10031)

Date: August 26, 2022

1 Design of a Ripple Carry Adder

A Ripple Carry Adder (RCA) is a circuit that adds two binary numbers. It is made out of a cascading series of Full Adders.

We begin by studying the simplest of adders: Half Adder.

(a) Half Adder Circuit

A Half Adder is a simple circuit which takes in two binary inputs a and b , and calculates their sum with a sum bit s and a carry bit c .

 


Figure 1: Circuit Diagram of Half Adder

a	b	s	c	Sum
0	0	0	0	00
0	1	1	0	01
1	0	1	0	01
1	1	0	1	10

Table 1: Truth Table of Half Adder



Figure 2: Simulation of Half Adder

(b) Full Adder Circuit

A Full Adder builds upon the design of a Half Adder by also considering a carry-in bit as input. Hence it takes three inputs a , b and c_0 , calculates their sum into a sum bit s and carry bit c .

 


Figure 3: Circuit Diagram of Full Adder

a	b	c_0	s	c	Sum
0	0	0	0	0	00
0	0	1	1	0	01
0	1	0	1	0	01
0	1	1	0	1	10
1	0	0	1	0	01
1	0	1	0	1	10
1	1	0	0	1	10
1	1	1	1	1	11

Table 2: Truth Table of Full Adder

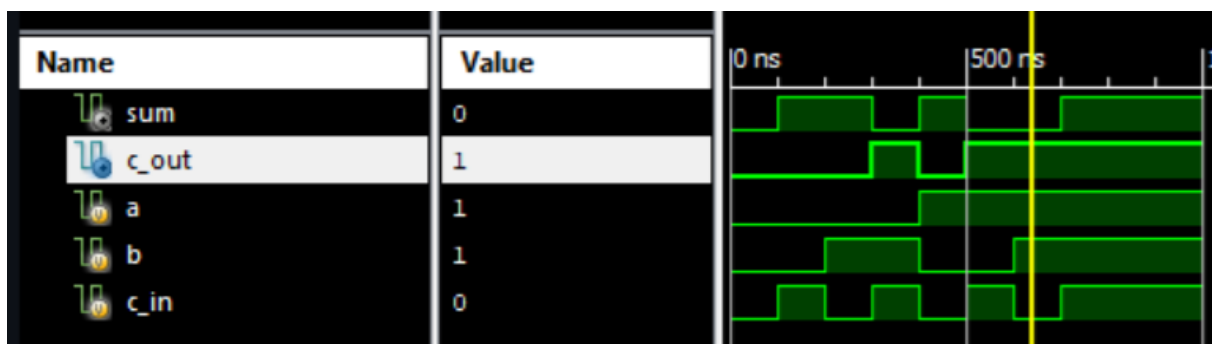


Figure 4: Simulation of Full Adder

(c) Ripple Carry Adder using Full Adders

Ripple Carry Adders can add N-bit binary numbers using a series of N Full Adders. The carry bit of each adder cascades (or ripples) to the next adder.

(i) 8-bit RCA

 


Figure 5: Circuit Diagram

 


Figure 6: Simulation of 8-bit RCA

Maximum combinational path delay: **3.471 ns**

(ii) 16-bit RCA

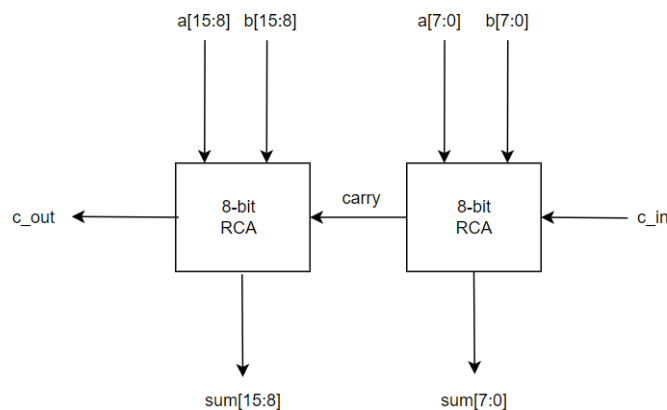


Figure 7: Circuit Diagram

Maximum combinational path delay: **6.167 ns**

 


Figure 8: Simulation of 16-bit RCA

(iii) 32-bit RCA

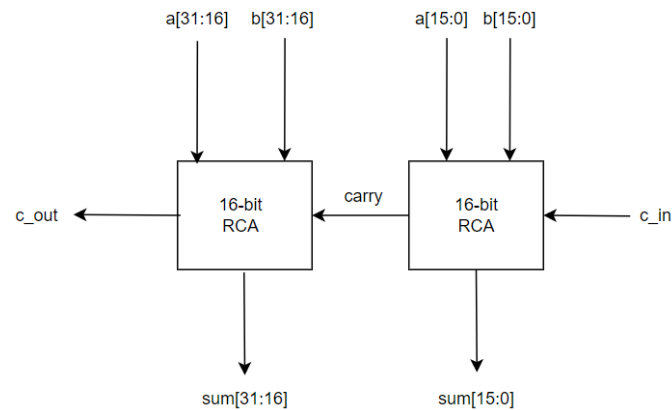


Figure 9: Circuit Diagram

 


Figure 10: Simulation of 32-bit RCA

Maximum combinational path delay: **11.559 ns**

(iv) 64-bit RCA

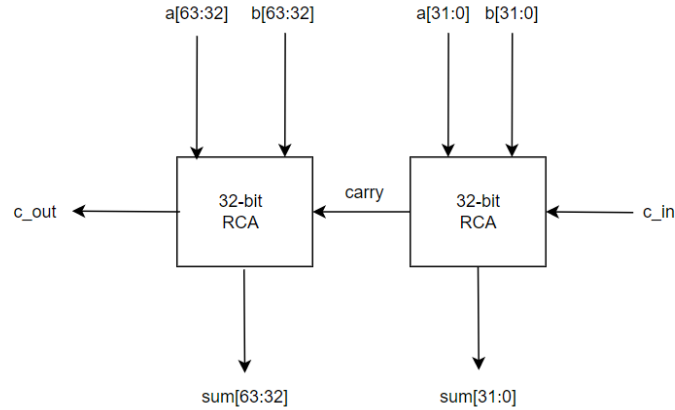


Figure 11: Circuit Diagram

 


Figure 12: Simulation of 64-bit RCA

Maximum combinational path delay: **22.343 ns**

(d) Subtraction using RCA

To calculate $a - b$, the idea is to add the 2's complement of b to a with an RCA. To get 2's complement of b , we first flip the bits of b to get \bar{b} . Next we set c_{in} of the adder to 1. This will transform b to $\bar{b} + 1$ which is the 2's complement of b . Finally we feed a , \bar{b} , and 1 (as c_{in}) to the RCA. This will yield the desired result.